

# ELL201 LAB PROJECT SERIAL GENERATOR

Aditya Agrawal  
2021AM10198

21 April 2023

## Contents

<b>1</b>	<b>Aim</b>	<b>2</b>
<b>2</b>	<b>State Diagram</b>	<b>2</b>
<b>3</b>	<b>State Table</b>	<b>2</b>
<b>4</b>	<b>Karnaugh Maps</b>	<b>3</b>
<b>5</b>	<b>Verilog Code</b>	<b>5</b>
<b>6</b>	<b>Test Bench Waveforms</b>	<b>6</b>

## 1 Aim


To design a sequence generator that generates the serial sequence:

$$X_3 = 9 \Rightarrow X_3 \% 8 = 1$$

$$X_4 = 8 \Rightarrow X_4 \% 8 = 0$$

$\therefore$  Serial Sequence :  $\{0,0,1,0,0,0\}$

## 2 State Diagram

 

State diagram of Mealy FSM after reduction

Here, 000 is the idle state. Since there are 6 states after reduction, we will need  $\geq \log_2 6$ , i.e., 3 flip-flops for the generator.

## 3 State Table

Current State			Input X	Output Y	Next State			D Flip-Flop		
$Q_{2n}$	$Q_{1n}$	$Q_{0n}$			$Q_{2n+1}$	$Q_{1n+1}$	$Q_{0n+1}$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	1	0	0	1	0
0	1	0	0	1	0	1	1	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	0	1	0	0	1	0	0
0	1	1	1	0	1	0	0	1	0	0
1	0	0	0	0	1	0	1	1	0	1
1	0	0	1	0	1	0	1	1	0	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

## 4 Karnaugh Maps

**K-Map for  $D_0$**

		$Q_{0_n} X$			
		00	01	11	10
$Q_{2_n} Q_{1_n}$	00	0	1	0	0
	01	1	1	0	0
	11	0	0	0	0
	10	1	1	0	0

**K-Map for  $D_1$**

		$Q_{0_n} X$			
		00	01	11	10
$Q_{2_n} Q_{1_n}$	00	0	0	1	1
	01	1	1	0	0
	11	0	0	0	0
	10	0	0	0	0

### K-Map for $D_2$

		$Q_{0_n} X$			
		00	01	11	10
$Q_{2_n} Q_{1_n}$	00	0	0	0	0
	01	0	0	1	1
	11	0	0	0	0
	10	1	1	0	0

### K-Map for $Y$

		$Q_{0_n} X$			
		00	01	11	10
$Q_{2_n} Q_{1_n}$	00	0	0	0	0
	01	1	1	0	0
	11	0	0	0	0
	10	0	0	0	0

Here,  $Q_0$  is the LSB and  $Q_2$  is the MSB. The states are represented by  $Q_2 Q_1 Q_0$ .

Here,  $D_0$  is the LSB and  $D_2$  is the MSB.

$$D_0 = Q_2 Q_1' Q_0' + Q_2' Q_1 Q_0' + Q_2' Q_0' X$$

$$D_1 = Q_2' Q_1' Q_0 + Q_2' Q_1 Q_0'$$

$$D_2 = Q_2' Q_1 Q_0 + Q_2 Q_1' Q_0'$$

$$Y = Q_2' Q_1 Q_0'$$

## 5 Verilog Code

```
module OIO(input d,input clk,output reg out);

always@(posedge clk)
begin
if (d==0) begin
out<=0;
end else if (d==1) begin
out<=1;
end
end
endmodule
```

Figure 1: Positive edge triggered D Flip-Flop

```
module fsm;
reg clk;
reg dc,db,da,x;
wire [2:0] q;
wire out;
assign out = ~q[2] & q[1] & ~q[0];
OIO df1(dc,clk,q[2]);
OIO df2(db,clk,q[1]);
OIO df3(da,clk,q[0]);
always @(posedge clk) begin
dc = (((q[2])&&(~q[0]))||((q[1])&&(q[0])));
db = (((q[1])&&(~q[0]))||((~q[2])&&(~q[1])&&(q[0])));
da = ((~q[0])&&(x||q[2]||q[1]));
end
initial begin
$dumpfile("fsm.vcd");
$dumpvars(0,fsm);
$monitor($time," %b Input = %b Output = %b State = %b
%b %b",clk,x,out,q[2],q[1],q[0]);
x = 0;
dc = 0;
db = 0;
da = 0;
clk = 1;
#7
x = 1;
#8
x = 0;
#20
x = 1;
#8
x = 0;
#20
$finish;
end
always #2 clk = ~clk;
endmodule
```

Figure 2: Mealy Implementation using 3 D Flip-Flops

```

# KERNEL:          0 1 Input = 0 Output = 0 State = 0 0 0
# KERNEL:          2 0 Input = 0 Output = 0 State = 0 0 0
# KERNEL:          4 1 Input = 0 Output = 0 State = 0 0 0
# KERNEL:          6 0 Input = 0 Output = 0 State = 0 0 0
# KERNEL:          7 0 Input = 1 Output = 0 State = 0 0 0
# KERNEL:          8 1 Input = 1 Output = 0 State = 0 0 0
# KERNEL:         10 0 Input = 1 Output = 0 State = 0 0 0
# KERNEL:         12 1 Input = 1 Output = 0 State = 0 0 1
# KERNEL:         14 0 Input = 1 Output = 0 State = 0 0 1
# KERNEL:         15 0 Input = 0 Output = 0 State = 0 0 1
# KERNEL:         16 1 Input = 0 Output = 0 State = 0 0 1
# KERNEL:         18 0 Input = 0 Output = 0 State = 0 0 1
# KERNEL:         20 1 Input = 0 Output = 1 State = 0 1 0
# KERNEL:         22 0 Input = 0 Output = 1 State = 0 1 0
# KERNEL:         24 1 Input = 0 Output = 1 State = 0 1 0
# KERNEL:         26 0 Input = 0 Output = 1 State = 0 1 0
# KERNEL:         28 1 Input = 0 Output = 0 State = 0 1 1
# KERNEL:         30 0 Input = 0 Output = 0 State = 0 1 1
# KERNEL:         32 1 Input = 0 Output = 0 State = 0 1 1
# KERNEL:         34 0 Input = 0 Output = 0 State = 0 1 1
# KERNEL:         35 0 Input = 1 Output = 0 State = 0 1 1
# KERNEL:         36 1 Input = 1 Output = 0 State = 1 0 0
# KERNEL:         38 0 Input = 1 Output = 0 State = 1 0 0
# KERNEL:         40 1 Input = 1 Output = 0 State = 1 0 0
# KERNEL:         42 0 Input = 1 Output = 0 State = 1 0 0
# KERNEL:         43 0 Input = 0 Output = 0 State = 1 0 0
# KERNEL:         44 1 Input = 0 Output = 0 State = 1 0 1
# KERNEL:         46 0 Input = 0 Output = 0 State = 1 0 1
# KERNEL:         48 1 Input = 0 Output = 0 State = 1 0 1
# KERNEL:         50 0 Input = 0 Output = 0 State = 1 0 1
# KERNEL:         52 1 Input = 0 Output = 0 State = 0 0 0

```

Figure 3: Output

## 6 Test Bench Waveforms

 


Figure 4: Generated Waveform